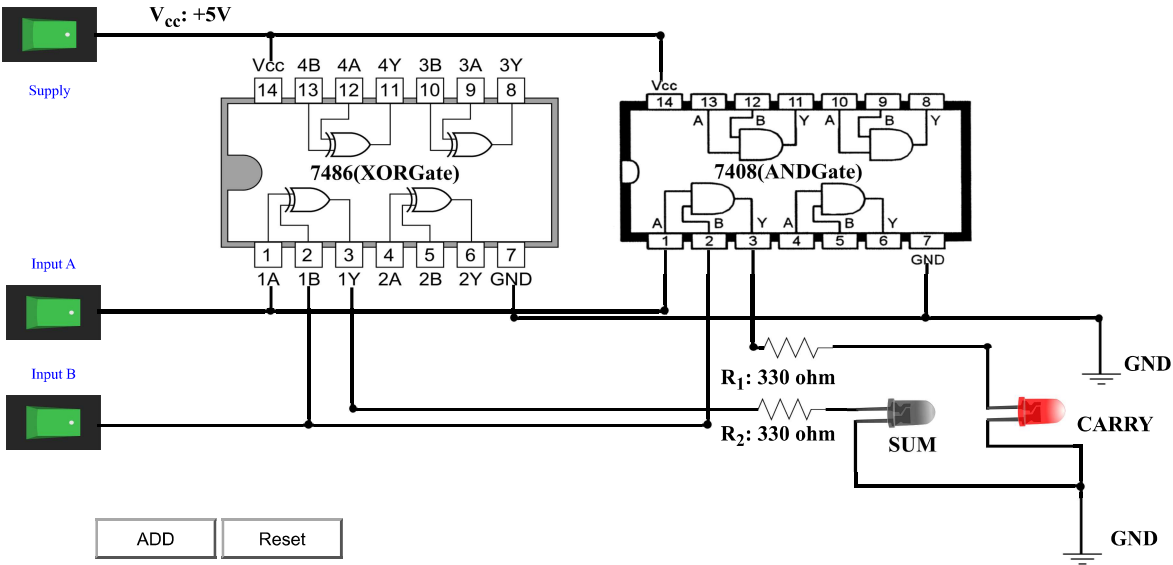


INSTRUCTIONS

Experiment to perform logic of half adder on kit



ADD Reset

TRUTH TABLE					Print
Serial No.	Input A	Input B	Sum	Carry	
1	0	0	0	0	
2	1	0	1	0	
3	0	1	1	0	
4	1	1	0	1	